

# Laboratory Exercise 2

## Numbers and Displays


This is an exercise in designing combinational circuits that can perform binary-to-decimal number conversion and binary-coded-decimal (BCD) addition.

### Part I

We wish to display on the 7-segment displays *HEX7* to *HEX0* the values set by the switches *SW<sub>15-0</sub>*. The objective of this task is to implement and verify the BCD (Binary-Coded Decimal) to Decimal conversion using the Nexys 4 DDR FPGA development board. You will design a digital circuit that takes a 4-bit BCD input and converts it to its corresponding decimal value, displaying the result on **one seven-segment display (HEX0)** of the Nexys 4 DDR kit. Your circuit should be able to display the digits from **0 to 9** and should treat the valuations 1010 to 1111 as don't-cares.

Truth table for common cathode type BCD to seven segment decoder


Decimal Digit	Input lines				Output lines							Display pattern
	A	B	C	D	a	b	c	d	e	f	g	
0	0	0	0	0	1	1	1	1	1	1	0	0
1	0	0	0	1	0	1	1	0	0	0	0	1
2	0	0	1	0	1	1	0	1	1	0	1	2
3	0	0	1	1	1	1	1	1	0	0	1	3
4	0	1	0	0	0	1	1	0	0	1	1	4
5	0	1	0	1	1	0	1	1	0	1	1	5
6	0	1	1	0	1	0	1	1	1	1	1	6
7	0	1	1	1	1	1	1	0	0	0	0	7
8	1	0	0	0	1	1	1	1	1	1	1	8
9	1	0	0	1	1	1	1	1	0	1	1	9

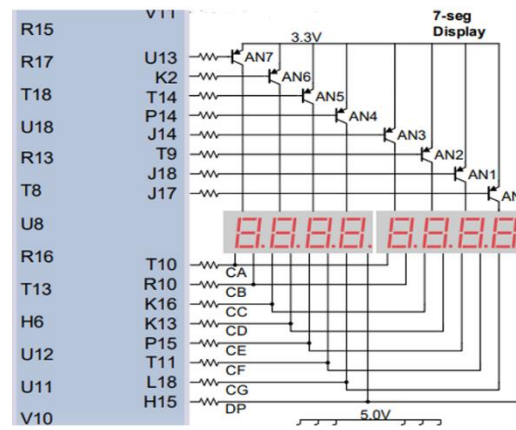

1. Create a new project which will be used to implement the above truth table on the Nexys 4 DDR FPGA board. The intent of this exercise is to manually derive the logic functions needed for the 7-segment displays. You should use only simple **Verilog case statements** in your code and specify each logic function as a Boolean expression.
2. Write a Verilog code that provides the necessary functionality. Include this code in your project and assign the pins on the FPGA to connect to the switches and 7-segment displays, as indicated in the above snap of 7-seg display of Nexys 4 DDR FPGA.
3. Compile the project and download the compiled circuit into the FPGA chip.
4. Test the functionality of your design by toggling the switches and observing the displays.
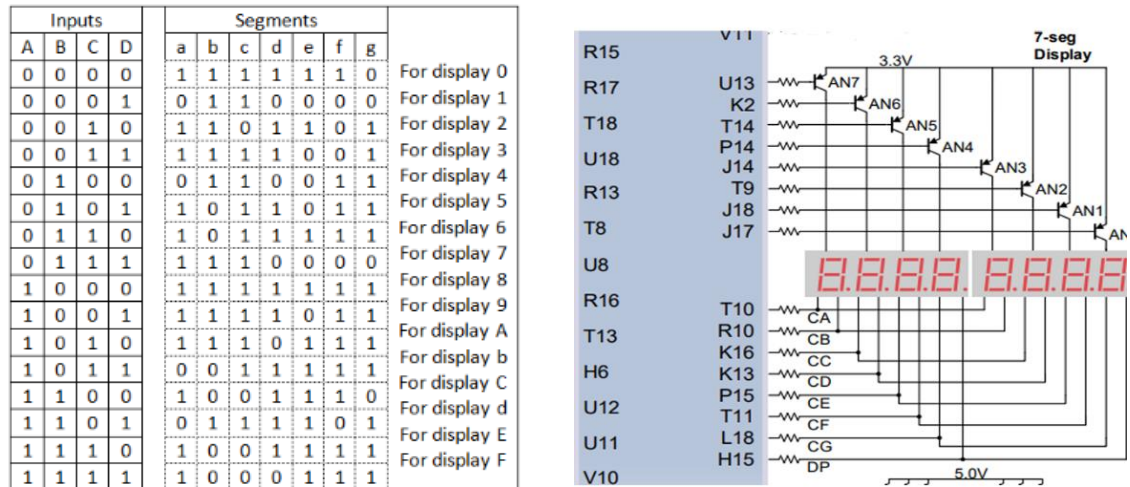
## Part II


We wish to display on the 7-segment displays *HEX7* to *HEX0* the values set by the switches  $SW_{15-0}$ . The objective of this lab task is to design, implement, and verify a Binary Coded Decimal (BCD) to Hexadecimal conversion circuit on the Nexys 4 DDR FPGA development board. You will create a digital circuit that takes a 4-bit BCD input, converts it to its corresponding Hexadecimal value, and displays the result on two seven-segment display (**HEX1**, **HEX2**) of the Nexys 4 DDR kit. Your circuit should be able to display the digits from **0 to F** and should treat the valuations above 1111 as don't-cares.




1. Create a new project which will be used to implement the above truth table on the Nexys 4 DDR FPGA board. The intent of this exercise is to manually derive the logic functions needed for the 7-segment displays. You should use only simple **Verilog case statements** in your code and specify each logic function as a Boolean expression.
2. Write a Verilog code that provides the necessary functionality. Include this code in your project and assign the pins on the FPGA to connect to the switches and 7-segment displays, as indicated in the above snap of 7-seg display of Nexys 4 DDR FPGA.
3. Compile the project and download the compiled circuit into the FPGA chip.
4. Test the functionality of your design by toggling the switches and observing the displays.

### Part III

Figure 2a shows a circuit for a *full adder*, which has inputs  $a$ ,  $b$ , and  $c_i$ , and produces the outputs  $s$  and  $c_o$ . Parts  $b$  and  $c$  of the figure show a circuit symbol and truth table for the full adder, which produces the two-bit binary sum  $c_o s = a + b + c_i$ . Figure 2d shows how four instances of this full adder module can be used to design a circuit that adds two four-bit numbers. This type of circuit is usually called a *ripple-carry* adder, because of the way that the carry signals are passed from one full adder to the next. Write a Verilog code that implements this circuit, as described below.

 


a) Full adder circuit

 

b) Full adder symbol

$b$	$a$	$c_i$	$c_o$	$s$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

c) Full adder truth table

 

d) Four-bit ripple-carry adder circuit

Figure 2. A ripple-carry adder circuit.

1. Create a new Vivado project for the adder circuit. Write a Verilog module for the full adder subcircuit and write a top-level Verilog module that instantiates four instances of this full adder.
2. Use switches  $SW_{7-4}$  and  $SW_{3-0}$  to represent the inputs  $A$  and  $B$ , respectively. Use  $SW_8$  for the carry-in  $c_{in}$  of the adder. Connect the  $SW$  switches to their corresponding red lights LEDR, and connect the outputs of the adder,  $c_{out}$  and  $S$ , to the green lights LEDG.
3. Include the necessary pin assignments for the NEXYS 4 DDR board, compile the circuit, and download it into the FPGA chip.
4. Test your circuit by trying different values for numbers  $A$ ,  $B$ , and  $c_m$ .